



Welcome to The Hardware Lab!

Fall 2016

Lab 5: Advanced Design Problems

Prof. Chun-Yi Lee

**Department of Computer Science
National Tsing Hua University**

Verilog Lab 5

- **Three basic questions (50%)**
 - Demonstration on **12/8/2016 (Thu), in class**
 - Report due on **12/13/2016 (Tue)**
- **Lab 5 report (30%)**
 - **Circuit or block diagram, and FSM state transition diagram** of your design, **and explain how it works**
 - Answer the questions listed in the handout (if any)
 - Contribution of each team member
 - What you have learned from Lab 5
- **Two optional questions (20%)**
 - Challenge it if you have extra time
 - Include in your Lab 5 report if you can make it
 - **Describe your design and how it works**

Verilog Lab 5 Rules


- You can use **ANY** modeling techniques
- Demonstrate your work by **waveforms (Q1~Q3)** and **FPGA (OQ1~OQ2)**
- Please follow the **module names** and **I/O ports** of the provided templates
 - Submit **only one testbench file** and **one design file**
 - **Avoid commenting out** modules in your submitted Verilog files
 - **Please keep in mind that we will deduct points if the module names and I/O port mismatch with the template**
- If not specifically mentioned, we assume the following SPEC
 - **CLK** is **positive edge triggered**
 - Reset the Flip-Flops when **RESET == 1'b0**

Verilog Lab 5 Submission

- **Demonstration and code** submission due date & time:
5:30pm, 12/8/2016 (Thu)
This is a HARD deadline
- **Report** submission due date & time:
5:30pm, 12/13/2016 (Tue)
This is a HARD deadline
- Please submit your report and Verilog codes to **ILMS**
 - Format: **Lab5_Team1_Codes.v, Lab5_Team1_Tb.v, Lab5_Team1_Report.pdf**
 - **We will deduct points if the submitted files mismatch the requirements**
 - **Please don't uncomment the modules in the template file**
- We will test your codes by our own testbench


Question 1

- **Mealy machine sequence detector**
 - 1-bit input **In** and 1-bit output **Dec**
 - When the four bit sequence is either **1100** or **1111**, **Dec** is set to 1
 - Re-detect the sequence **every four bits**
 - Please draw your state diagram in your report

 

Question 2


- **Sliding Window** sequence detector
 - **Dec1** == 1'b1 when input is **101** AND no **111** occurs before
 - **Dec2** == 1'b1 when input sequence is **0110**
- **Continuous detection**
 - Detect the sequences whenever they occur
 - Please draw a state transition diagram in your report

 

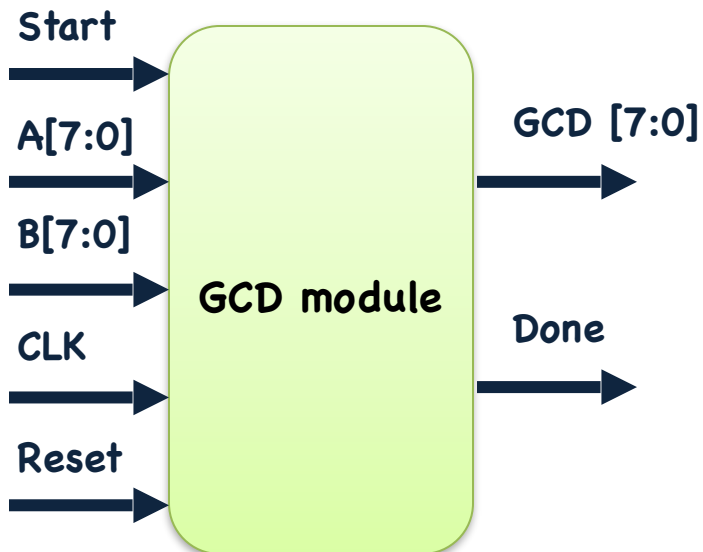Question 3

Greatest Common Divisor (GCD)

- Calculate the greatest common divisor of two numbers **A** and **B**
- Block diagram and pseudo code are as follow
 - You **shall not** use **while statements** in your Verilog codes



Function gcd (a, b)

begin

if (a == 0)
return b;

while (b != 0)

// Do the following operation once per clock cycle

begin

if (a > b)
a = a - b;

else
b = b - a;

end

return a;


end

**GCD pseudo
code**

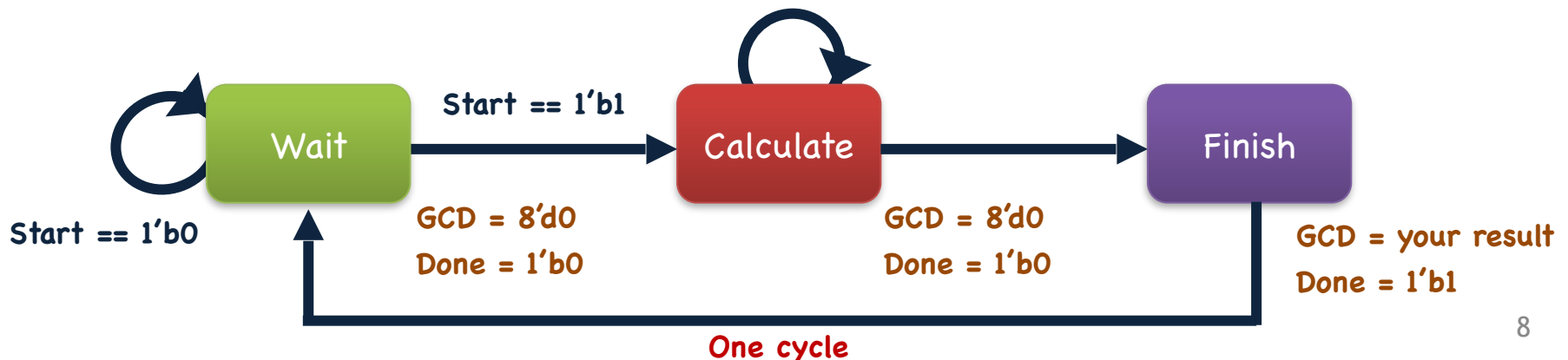Question 3 (Cont'd)

Greatest Common Divisor (GCD)

- Three states are used: **Wait**, **Calculate**, and **Finish**
- **Wait state**
 - Wait for $\text{Start} == 1'b1$ (**one cycle**) to begin the operation
 - When $\text{Reset} == 1'b0$, reset the module to the **Wait state**
- **Calculate state**
 - Calculate the **subtraction operations once per cycle**
- **Finish state**
 - Output the GCD result for **one cycle**
 - $\text{Done} == 1'b1$ for **one cycle**



Optional Question 1

Vending Machine

- Four options available: **Coffee**, **Coke**, **Oolong**, and **Milk Tea**
 - Prices are: **Coffee (NT\$ 40)**, **Coke (NT\$ 15)**, **Oolong (NT\$ 20)**, **Milk Tea (NT\$ 30)**
- The **two rightmost 7-segment** displays show the money inserted into the machine
 - When RESET == 1'b0, please display "00"
 - The maximum value is **NT\$ 70**
- Use **three buttons** to insert money
 - You can insert **NT\$ 5**, **NT\$ 10**, and **NT\$ 50**



Optional Question 1 (Con'd)

Vending Machine

- Use **four LEDs** to indicate which drinks you can buy
 - **LED[3:0]** corresponds to Coffee, Coke, Oolong, and Milk Tea, respectively
- Use **four Switches** to buy a drink
 - **SW[3:0]** corresponds to Coffee, Coke, Oolong, and Milk Tea, respectively
 - You can only buy one drink at a time
- Use the **two rightmost 7-segment display** to show the change after buying a drink
 - E.g., if you inserted **NT\$ 40** and bought a can of Coke (**NT\$ 15**), the 7-segment display will show **NT\$ 25**

Optional Question 1 (Con'd)

Vending Machine

- Assume that the machine allows you to buy **ONLY ONE DRINK** at a time
- Decrement the **7-segment display** by **NT\$ 5** every second to mimic the process of returning changes
 - Return the changes until it becomes zero
- If the buyer does not want to buy a drink, he/she can use a **cancel button** to cancel it
 - The inserted money will be returned the same way (**NT\$ 5** per second)

The layout of the
buttons used in this
question



Insert NT
\$ 5



RESET



Insert NT
\$ 10



Insert NT
\$ 50




Cancel

Optional Question 2

Calculator

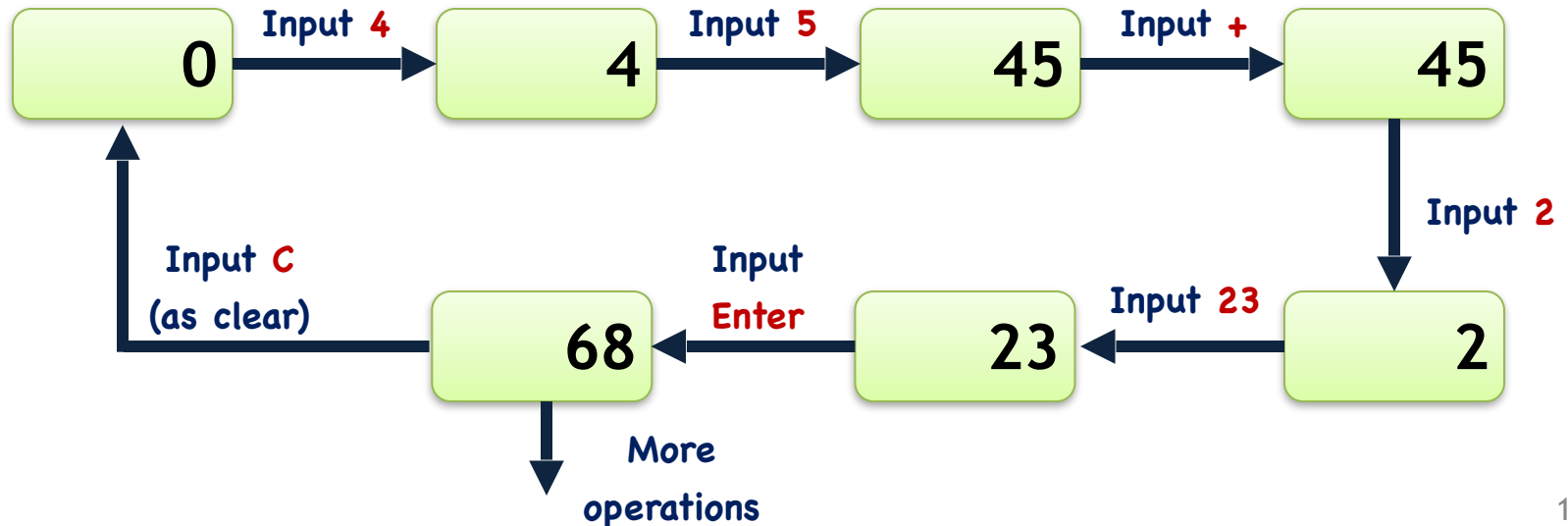- Please use your keyboard to implement a calculator
 - The calculator can perform **+**, **-**, and **x**
 - To simplify your design, please use the letter **"x"** for multiplication operation
 - Use your keyboard to provide inputs
- The flow of the calculator is as follows:



Optional Question 2 (Cont'd)

Calculator

■ Clear

- Use the “**C**” key as clear
- **You can hit this clear anytime to reset the calculator to zero**

■ Overflow

- If the result is larger than **999** or less than **-999**, simply show **999** and **-999**

■ Cascade operations

- You can cascade your results with more operations
- E.g., You can continue with **+**, **-**, and **x** from the previous result **68** in the above example

Thank you for your attention!



*Lake Helen at Lassen Volcanic National Park, Shasta County, California, USA
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography